

CONTENTS



UNIVERSIDAD NACIONAL DE ENTRE RÍOS
FACULTAD DE INGENIERIA
CENTRO DE MEDIOS
BIBLIOTECA

Nº 1 400

Preface ix

1. OPTIMIZING OPERATIONAL AMPLIFIER PERFORMANCE.....	1
1.1 Preserving DC Performance	1
1.1.1 Thermal transient response of input offset voltage	2
1.1.2 Drift effects of input offset voltage nulling	3
1.1.3 Null techniques with no drift effect	6
1.1.4 Prediction of input current behavior	12
1.1.5 Input guarding	14
1.2 Preserving AC Performance	14
1.2.1 Optimizing gain accuracy	15
1.2.2 Operational amplifier response characteristics	17
1.2.3 The significance of input capacitance	21
1.3 Optimizing Noise Performance	25
1.3.1 Signal-to-noise ratio optimization	25
1.3.2 Noise-figure optimization	26
1.4 Overload Protection	28
1.4.1 Protection from power-supply faults	28
1.4.2 Input protection	29
1.4.3 Output protection	31

2. AMPLIFIERS	35
2.1 Increasing Input Impedance 35	
2.1.1 Input buffering 36	
2.1.2 Bootstrapping 38	
2.1.3 Isolation techniques 40	
2.2 Increasing Output Drive Capabilities 42	
2.2.1 Output current boosting 42	
2.2.2 Output voltage boosting 46	
2.2.3 Output power boosting 49	
2.3 Differential Output Amplifiers 50	
2.4 Instrumentation Amplifiers 53	
2.4.1 Simplified instrumentation amplifiers 53	
2.4.2 Input guarding 57	
2.4.3 Improving common-mode rejection 59	
2.4.4 A linear gain control 61	
2.5 Isolation Amplifiers 63	
2.5.1 Feedback linearized configurations 63	
2.5.2 Modulated carrier configurations 67	
3. SIGNAL CONDITIONERS	70
3.1 Integrators and Differentiators 70	
3.1.1 Specialized integrators 71	
3.1.2 Integrator reset 73	
3.1.3 Specialized differentiators 76	
3.2 Controlled Current Sources 78	
3.2.1 Unipolar output current sources 79	
3.2.2 Improving unipolar output characteristics 84	
3.2.3 Special-purpose unipolar current sources 86	
3.2.4 Bipolar output current sources for floating loads 89	
3.2.5 Bipolar output current sources for grounded loads 92	
3.3 Logarithmic Amplifiers 94	
3.3.1 Compensation of bulk resistance error 95	
3.3.2 Improving frequency response 96	
3.4 Multiplier/Dividers 97	
3.4.1 Voltage-controlled resistor techniques 97	
3.4.2 A logarithmic amplifier technique 100	
3.5 Active Filters 102	
3.5.1 Tunable active filters 102	
3.5.2 Removing dc offset 106	
4. SIGNAL PROCESSORS	109
4.1 Comparators 109	
4.1.1 Specialized comparators 110	
4.1.2 Simplified window comparators 112	
4.2 Multiplexers and Clamps 114	
4.2.1 Multiplexing amplifiers 114	
4.2.2 Clamping Amplifiers 118	

4.3	Absolute-value Circuits	119
4.3.1	Precision absolute-value circuits	120
4.3.2	Single amplifier configurations	125
4.3.3	Improving frequency response	129
4.4	Sample-hold and Peak Detector Circuits	132
4.4.1	Accuracy improvements	132
4.4.2	Speed improvements	136
4.5	RMS Converters	139
4.5.1	Computing techniques	139
4.5.2	Thermal techniques	141
5.	SIGNAL GENERATORS	144
5.1	Sine-wave Generators	144
5.1.1	Wien-bridge oscillators	145
5.1.2	Variable frequency circuits	148
5.1.3	Variable-amplitude circuits	151
5.2	Square- and Triangle-wave Generators	154
5.2.1	Single amplifier configurations	155
5.2.2	Variable circuits	158
5.3	Ramp and Pulse Generators	163
5.3.1	Single amplifier configurations	164
5.3.2	Other ramp and pulse generators	168
5.4	Monostable Multivibrators	171
5.5	Modulated Signal Generators	175
5.5.1	Amplitude-modulated generators	176
5.5.2	Frequency-modulated generators	177
5.5.3	Pulse width-modulated generators	180
6.	SPECIAL-PURPOSE CIRCUITS	183
6.1	Transistor Test Circuits	183
6.1.1	Gain measurement	184
6.1.2	Breakdown and leakage testing	186
6.1.3	Output resistance measurement	189
6.1.4	Noise measurement	192
6.1.5	Other transistor test circuits	194
6.2	Measurement Circuits	198
6.2.1	Meter circuits	198
6.2.2	Frequency and phase measurement circuits	200
6.2.3	Other measurement circuits	203
6.3	Controllers	205
6.3.1	On-off controllers	205
6.3.2	Proportional controllers	207
6.3.3	An optimizing controller	212
6.4	Other Special-purpose Circuits	214
6.4.1	Audio circuits	214
6.4.2	AGC circuits	217
	<i>Glossary</i>	221
	<i>Index</i>	227