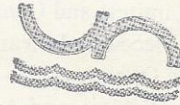


CONTENTS



UNIVERSIDAD NACIONAL DE ENTRE RÍOS
FACULTAD DE INGENIERIA
CENTRO DE MEDICOS
BIBLIOTECA

Nº 1 413

Preface	xi
1 Basic Operational Amplifier Circuits	1
1.1 General Characteristics of Operational Amplifiers	3
1.2 The Ideal Amplifier Model	3
1.3 The Summer-Inverter	7
1.4 The Inverting Summer-Integrator	12
1.5 The General Inverting Amplifier	23
1.6 The Noninverting Amplifier	27
1.7 The Differential Amplifier	31
1.8 The Combined Inverting and Noninverting Amplifier	34
1.9 Simple First-Order Transfer Functions	40
1.10 Miscellaneous Linear Applications	47
References and Bibliography	55
Problems	55
2 Performance Limitations: The Nonideal Amplifier	71
2.1 The General Nonideal Linear Model	73
2.2 Closed-Loop Gain, Output Impedance, and Input Impedance	76
2.3 Closed-Loop Stability; Bode Plot Methods; Compensation	91

2.4	Common-Mode Effects	96
2.5	DC Offsets and Temperature Drift	101
2.6	Amplifier Internal Noise Effects	107
2.7	Large-Signal Limitations	118
2.8	Output Power Boosting	121
2.9	Power Supplies, Grounding, and Shielding	124
2.10	Components: Resistors and Capacitors	128
	References and Bibliography	130
	Problems	130
3	Nonlinear Circuit Applications	141
3.1	General Nonlinear Design Approach	142
3.2	Feedback Limiters and Comparators	150
3.3	Additional Piecewise-Linear Functions	171
3.4	Logarithmic Operators	195
3.5	Multipliers, Dividers, and Applications	203
3.6	Waveform Generation	219
	References and Bibliography	236
	Problems	236
4	Active RC Filters	257
4.1	General Design and Evaluation Techniques—Sensitivity	258
4.2	Second-Order Low-Gain-Amplifier Filters	266
4.3	Second-Order Infinite-Gain-Amplifier Filters	278
4.4	High- Q Filters	289
4.5	Cascade Realization of High-Order Filters—Tuning	295
4.6	Gyrator Filters and Negative-Impedance Converters	307
4.7	Generalized Impedance Converter Filters	315
	References and Bibliography	323
	Problems	324
5	Electronic Switching Circuits	329
5.1	Introduction	329
5.2	Ideal Switches and Real Switching Circuits	330
5.3	Diode Switching Circuits	332
5.4	Bipolar-Transistor Switches	334
5.5	Junction Field-Effect Transistor (JFET) Switches	337
5.6	Metalized-Oxide-Semiconductor Field-Effect Transistor (MOSFET) Switches and CMOS Integrated Circuits	341
5.7	Some Improved Switching Circuits	344
5.8	Sample-Hold Circuits	345
5.9	Integrator Mode Control and Related Switching Circuits	349
	References and Bibliography	354

6	Digital-to-Analog and Analog-to-Digital Converters	357
6.1	Digital Representation of Voltages; Simple Conversion Circuits	357
6.2	Practical Digital-to-Analog Converters; Voltage-Ladder Circuits	360
6.3	Current-Switching DACs	371
6.4	Static-Error Specifications	373
6.5	A Discussion of DAC Settling Time; Spikes and Glitches	373
6.6	Analog-to-Digital Conversion	376
6.7	Parallel-Comparator and Cascade-Encoder ADCs	376
6.8	Ramp-Comparator Converters	380
6.9	Integrating Converters	380
6.10	Analog-to-Digital Converters Using Digital-to-Analog Feedback	382
6.11	Specifications and Comparison of Analog-to-Digital Converters	384
	References and Bibliography	387
	Problems	388
	Index	389



UNIVERSIDAD NACIONAL DE ENTRE RÍOS
 FACULTAD DE INGENIERIA
 CENTRO DE MEDIOS
 BIBLIOTECA