

Contents



UNIVERSIDAD NACIONAL DE ENTRE RÍOS
FACULTAD DE INGENIERIA
CENTRO DE MEDIOS
BIBLIOTECA

Nº 1 927

Preface	xiii
CHAPTER 1 / DIRECT CURRENT CIRCUITS	1
Introductory Concepts	2
Current, voltage, and resistance / Ohm's law / Joule's law	
Circuit Elements	4
Resistors / Batteries	
Simple Circuits	9
Series circuits / Parallel circuits / Networks	
Circuit Analysis	14
Kirchhoff's rules / Wheatstone bridge / Potentiometer circuit	
Equivalent Circuits	21
Thévenin's theorem / Norton's theorem / Maximum power transfer	
Electrical Measurements	26
D'Arsonval meter / Ammeters and voltmeters / Ohmmeters and multimeters	
Suggestions for Further Reading	32
Exercises	32

CHAPTER 2 / ALTERNATING CURRENTS	36
Sinusoidal Signals	37
Frequency, amplitude, and phase / Rms value / Power factor	
Capacitance and Inductance	40
Capacitive reactance / Capacitors / Inductive reactance / Inductors	
Simple Circuits	45
RL filter / RC filter / Differentiating and integrating circuits	
Transient Currents	51
Time constant / Ac transients / Ringing	
Complex Waveforms	58
Fourier series / Effective value / Square-wave response / Oscilloscope	
Suggestions for Further Reading	69
Exercises	70
CHAPTER 3 / AC-CIRCUIT ANALYSIS	71
Impedance	72
Ohm's law for ac / Complex impedance	
RLC Circuits	75
Series resonance / Parallel resonance / Q factor	
Bridge Circuits	82
Inductance and capacitance bridge / Wien bridge / Bridged-T and twin-T networks	
Transformers	90
Mutual inductance / Transformer ratio / Practical transformers	
Suggestions for Further Reading	94
Exercises	94
CHAPTER 4 / DIODE CIRCUITS	96
Nonlinear Components	97
Current-voltage characteristics / The ideal rectifier / The junction diode	
Rectifier Circuits	101
Half-wave rectifier / Full-wave rectifier / Bridge rectifier / Voltage doubler	
Filters	104
Capacitor filter / L-section filter / π -section filter	
Voltage Regulators	109
Zener diodes / Controlled rectifiers	

Diode Circuits	114
Clippers / Clamps / Ac voltmeters / Detectors	
Suggestions for Further Reading	121
Exercises	121

CHAPTER 5 / SEMICONDUCTOR DEVICES	123
Semiconductors	124
Energy bands / Electrons and holes / Extrinsic semiconductors	
Semiconductor Diodes	128
The <i>pn</i> junction / The tunnel diode / Minority carrier injection	
Junction Transistors	133
Collector characteristics / Silicon controlled rectifier / The unijunction transistor / Fabrication of transistors	
Field-Effect Transistors	143
Drain characteristics / The transfer characteristic / IGFETs and MOSFETs	
Integrated Circuits	150
Principles of integrated circuits / Fabrication processes / Practical circuits	
Suggestions for Further Reading	155
Exercises	155

CHAPTER 6 / TRANSISTOR AMPLIFIERS	156
The Operating Point	157
Load lines / Source bias / Small-signal parameters	
FET Amplifiers	165
Source follower / FET voltmeter / MOSFET amplifier	
Junction-Transistor Amplifier	169
Bias circuits / T-equivalent circuit / Hybrid parameters	
Junction-Transistor Circuits	176
Common emitter / Grounded base / Emitter follower / Difference amplifier	
Special Amplifiers	185
Complementary symmetry / Darlington connection / Integrated-circuit MOSFET	
Suggestions for Further Reading	187
Exercises	188

CHAPTER 7 / AMPLIFIER CIRCUITS	190
Voltage Amplifiers	191
Cascading / Low-frequency gain /	
High-frequency gain / Decoupling	
Power Amplifiers	199
Transformer coupling / Push-pull amplifier /	
Special circuits	
Tuned Amplifiers	207
Tuned coupling / Neutralization	
Pulse Amplifiers	211
Rise time / Tilt	
DC Amplifiers	214
Direct coupling / Chopper amplifiers / Lock-in	
amplifier	
Suggestions for Further Reading	223
Exercises	223
CHAPTER 8 / OPERATIONAL AMPLIFIERS	225
Negative Feedback	226
Voltage feedback / Current feedback / Stability	
Operational Feedback	234
The virtual ground / Mathematical operations /	
Simple amplifier	
Operational-Amplifier Circuits	238
Practical amplifiers / Integrator-differentiator	
circuit / Logarithmic amplifier / Active filter /	
Comparator	
Analog Computers	250
Simulation / Damped harmonic oscillator	
Suggestions for Further Reading	252
Exercises	252
CHAPTER 9 / OSCILLATORS	254
Positive Feedback	255
RC Oscillators	255
Phase-shift oscillator / Wien bridge oscillator	
Resonant-Circuit Oscillators	259
LC oscillators / Crystal oscillators	
Negative Resistance Oscillators	266
Stability analysis / Tunnel-diode oscillator	
Relaxation Oscillators	270
Sawtooth generators / Multivibrators	
Waveform Generators	284
Diode pump / Ramps / Pulses	

Suggestions for Further Reading	288
Exercises	288
CHAPTER 10 / ANALOG MEASUREMENTS	290
Control Circuits	291
Voltage regulators / Servos	
Transducers	299
Mechanical transducers / The pH meter / Photocells	
Analog Instruments	309
Oscilloscopes / Waveform analyzer / Magnetic recorder / Electrometer	
Noise Signals	317
Thermal noise / Current noise / Noise in transistors / Shielding and grounding	
Transmission Lines	323
Characteristic impedance / Delay time / Reflections and resonance / Waveguides	
Suggestions for Further Reading	331
Exercises	331
CHAPTER 11 / DIGITAL ELECTRONICS	334
Digital Logic	335
Binary numbers / Logic gates / Boolean Algebra	
Logic Circuits	344
Logic Signals / DTL, TTL, and ECL logic / ADD gates	
Information Registers	351
Flip-flops / Counters / Registers	
Visual Displays	361
Single-element displays / Seven-segment displays / Decoder logic	
Memory Circuits	369
Read-only memories / MOS Shift-register memories / Random-access memories	
Suggestions for Further Reading	377
Exercises	377
CHAPTER 12 / DIGITAL MEASUREMENTS	378
Digital Instruments	379
Time-interval meter / Frequency meter / Digital voltmeter	

A-D and D-A Conversion	382
Dual-slope integration / Successive- approximation converter / D-A ladder networks	
Digital Processors	387
Digital filter / Signal correlators / Transient recorder	
Digital Computers	393
Organization / Microcomputers / Programming languages	
Suggestions for Further Reading	399
Exercises	400
 APPENDIX / VACUUM-TUBE CIRCUITS	 402
The Vacuum Diode	403
Thermionic emission / Child's law	
Vacuum Tubes	405
The grid / Pentodes / Other multigrad tubes	
The Triode Amplifier	411
Cathode bias / Small-signal parameters / Triode equivalent circuit	
 Index	 419