

Contents

UNIVERSIDAD NACIONAL DE
FACULTAD DE INGENIERIA
CENTRO DE MEDIOS
BIBLIOTECA

Preface	xiii
List of Frequently Used Symbols	xvi
Prefixes for Units	xviii
1. Signal Sources and Signal Processing	1
1.1 Reference conventions for signals	1
1.2 Models of signal sources and notation	5
1.3 Nature of signal processing in networks	12
1.4 Summary	17
Problems	18
2. Signal Waveforms	21
2.1 The exponential function	21
2.2 The step, ramp, and impulse	24
2.3 The sinusoid	29
2.4 Three-phase sinusoidal sources	34
2.5 Sampled signals and quantized signals	35

2.6 Signals with time delay	36
2.7 Summary	40
Problems	42
3. Partial Signal Specifications	46
3.1 Average value of a signal	46
3.2 Peak value of a signal	50
3.3 Root-mean-square value of a signal	51
3.4 Specification of the response to a step input	54
3.5 The measurement of signal characteristics	57
3.6 Summary	57
Problems	58
4. Network Models for Devices	60
4.1 Terminal properties of R , L , and C elements	60
4.2 Voltage–current relationships for magnetically coupled coils	69
4.3 Ideal converters	72
4.4 Operational amplifiers	75
4.5 Summary	80
Problems	81
5. Kirchhoff's Laws	85
5.1 Network terminology	85
5.2 Kirchhoff's current law	86
5.3 Kirchhoff's voltage law	89
5.4 Applications to simple networks	91
5.5 Choice of network variables	97
5.6 Summary	101
Problems	102
6. Energy and Power	107
6.1 Energy dissipation and energy storage in network elements	107
6.2 Average power for periodic signals	109

6.3	Passive, active, and lossless networks	111
6.4	Conservation of energy	113
6.5	Tellegen's theorem	118
*6.6	Energy considerations in a network with nonlinear elements	121
6.7	Summary	129
	Problems	130
7.	Implications of Linearity in Networks	136
7.1	Characteristics of a linear system	136
7.2	The Thevenin and Norton theorems	143
7.3	Time-invariant systems	153
7.4	Linear time-invariant differential systems	155
7.5	Stability of linear networks	163
7.6	Summary	169
	Problems	171
8.	Further Implications of Linearity : Convolution and Impulse Response	179
8.1	Simple application of linearity and time-invariance	179
8.2	The convolution integral	183
8.3	Graphical interpretation of convolution	188
8.4	Impulse response from differential equations	191
8.5	Total solution by decomposition property	197
8.6	Total solution using the particular integral	201
8.7	Summary	207
	Problems	208
9.	Phasors for Sinusoidal Steady-state Analysis	214
9.1	Addition of sinusoids of the same frequency	215
9.2	Complex-number arithmetic	216
9.3	Phasors and rotating phasors	221

9.4 Steady-state response to $e^{j\omega t}$	225
9.5 Summary	228
Problems	230
10. The Impedance Concept and Network Functions	234
10.1 Impedance for sinusoidal signals	234
10.2 Impedance of R , L , and C elements	237
10.3 The impedance of series-parallel networks	240
10.4 Analysis with phasor diagrams	247
10.5 Complex power	250
10.6 Generalization of impedance: network functions	258
10.7 Network functions for signals of the form Ke^{st}	261
10.8 Thevenin's and Norton's theorems again	265
10.9 Summary	269
Problems	271
11. Resonance and Signal Filtering	278
11.1 Filtering	278
11.2 Series resonance	282
11.3 Parallel resonance	288
11.4 Locus diagrams	292
11.5 Locus of roots	296
11.6 Magnitude and phase functions from pole-zero diagrams	301
11.7 Summary	304
Problems	305
12. Linear Independence of Topological Equations	312
12.1 Linearly independent variables and equations	312
12.2 Network topology	315
12.3 Number of independent topological constraints	319
12.4 Choosing independent equilibrium equations	322

12.5 Choosing network variables 328

12.6 Summary 332

Problems 332

13. Loop, Node, and State Equations 336

13.1 Formulation of linear time-invariant network equations on the node basis 336

13.2 Formulation of linear time-invariant network equations on the loop basis 344

13.3 Linear time-invariant networks with mixed sources 350

13.4 State-variable method 356

13.5 Summary 364

Problems 364

14. Determination of Solutions for Linear Time-invariant Networks 379

14.1 Gauss's elimination method 379

14.2 Cramer's rule 385

14.3 Simultaneous differential equations 389

14.4 Summary 394

Problems 395

15. Terminals and Ports 398

15.1 Classes of networks: breadboards and black boxes 398

15.2 Two-port parameters 402

15.3 Two-port reciprocity 412

15.4 Linear incremental models for some electronic 2-ports 417

15.5 Summary 422

Problems 423

16. Three-phase Power Networks 429

16.1 Balanced Y - Y systems 430

16.2 Δ - Y transformations 436

16.3	Balanced Y - Δ systems	439	
16.4	Unbalanced three-phase systems	443	
16.5	Two-wattmeter method	445	
16.6	Simple load-flow analysis	448	
16.7	Summary	452	
	Problems	453	
17.	Fourier Series		456
17.1	Sums of exponential signals	456	
17.2	The Fourier coefficients	461	
17.3	Signal symmetry	469	
17.4	Truncation and least mean-square error property of Fourier series	474	
17.5	Summary	480	
	Problems	482	
18.	Transforms and Spectra		487
18.1	Exponential Fourier series	487	
18.2	Discrete signal spectra	491	
18.3	Steady-state response to periodic signals	495	
18.4	Introduction to the Fourier transform	500	
18.5	Spectra and steady-state response again	508	
18.6	An introduction to the Laplace transform	512	
18.7	Summary	518	
	Problems	520	
Appendix A.	Network Models for Mechanical Devices and Systems		525
A.1	Linear mechanical elements	525	
A.2	D'Alembert's principle	530	
A.3	Summary	534	
A.4	Collateral reading references	534	

Appendix B. Digital Computer Exercises	535
B.1 Basic computational problems	536
B.2 Network and system-oriented computational problems	536
B.3 References	538
Appendix C. The Laplace Transform	540
C.1 Definition	540
C.2 Table of transforms	540
C.3 Transforms of integro-differential equations	542
C.4 Additional properties of the Laplace transform	544
C.5 Partial-fraction expansion	545
C.6 Network analysis by the Laplace transform method	549
C.7 Summary	550
C.8 Collateral reading references	551
Appendix D. The Newton–Raphson Method	554
Appendix E. References	558
E.1 Collateral reading	558
E.2 Intermediate-level textbooks	559
E.3 Device modeling	559
E.4 Historical interest	560
E.5 Computer-oriented analysis	560
Answers to Exercises	562
Index	590