

# CONTENTS

---

<b>1. INTRODUCTION TO ELECTRONIC WAVEFORMS</b>	<b>1</b>
1.1. Analog and Digital Signals Produced by Different Circuits	1
1.2. Sinusoidal Waveform	4
1.3. Pulse-Waveform Characteristics	5
1.4. Sawtooth Waveform Produced by a Basic Ramp Generator	7
1.5. Frequency-Modulated (FM) Waveform	8
1.6. Pulse-Amplitude-Modulated (PAM) Waveform	10
1.7. Harmonic Content of Sawtooth and Square Waveforms	12
<b>2. THEORY AND APPLICATION OF LINEAR WAVESHAPING CIRCUITS</b>	<b>18</b>
2.1. RC Network with Sine-Wave Input	18
2.2. RC Network with Step-Function (Step-Voltage) Input	22
2.3. RC Network with Pulse Input	23
2.4. RC Network with Square-Wave Input	25
2.5. RC Network with Exponential Input	29
2.6. The RC Network Used as a Basic Exponential Pulse Generator	33
2.7. RC Network with Ramp Input	33
2.8. RC Differentiators and Integrators	37
2.9. RC Differentiator and Integrator Used for Separation of Horizontal and Vertical Sync Pulses in a TV Receiver	43

**viii CONTENTS**

- 2.10. Compensated Attenuators 44
- 2.11. *RL* and *RLC* Circuits 47
- 2.12. Pulse Transformers 52
- 2.13. Delay Lines 59
- 2.14. Laplace Transforms Applied to Linear Network Analysis 65

**3. THEORY AND APPLICATION OF SEMICONDUCTOR-DIODE SWITCHING**

**83**

- 3.1. Steady-State Switching Characteristics of pn-Junction Diodes 83
- 3.2. Diode Clippers 87
- 3.3. Diode Clampers 94
- 3.4. IC Diode Array 102
- 3.5. Diode-Switching Counters 105
- 3.6. Dual-Diode Sync Discriminators for Horizontal AFC in TV Receivers 107
- 3.7. Two Basic Diode Logic Gates 112
- 3.8. Junction Diode Transient Characteristics 115

**4. TRANSISTOR SWITCHING**

**121**

- 4.1. Three Operation Regions of Bipolar-Transistor Characteristics 121
- 4.2. Application of Ebers-Moll Equations to Bipolar-Transistor Characteristics 129
- 4.3. Bipolar-Transistor Inverter and Its Load 135
- 4.4. Bipolar-Transistor Switching Times and Switching Speed Improvement 139
- 4.5. Junction Field-Effect Transistors (JFETs) 144
- 4.6. Metal-Oxide-Semiconductor FETs (MOSFETs) 147
- 4.7. JFET and MOSFET Switches 149
- 4.8. CMOS Switches 151

**5. TRANSISTOR AND IC COMPARATOR CIRCUITS**

**156**

- 5.1. Introduction to Comparators 156
- 5.2. A Transformer-Coupled Regenerative Comparator 157
- 5.3. Operation of Transistor Schmitt Trigger Circuit 159

5.4.	Schmitt Trigger Circuit Analysis	162	
5.5.	Design of Transistor Schmitt Trigger Circuits	167	
5.6.	Schmitt Trigger Integrated Circuits	170	
5.7.	IC Op-Amps as Schmitt Trigger Circuits	171	
5.8.	IC 710 High-Speed Differential Comparator as Schmitt Trigger Circuit	179	
5.9.	IC Op-Amps as Voltage Comparators	181	
<b>6.</b>	<b>ASTABLE AND MONOSTABLE MULTIVIBRATORS AND BLOCKING OSCILLATORS</b>		<b>189</b>
6.1.	Transistor Astable Multivibrator Circuits	189	
6.2.	Emitter-Coupled Astable Multivibrator as Horizontal Oscillator in a Television Receiver	195	
6.3.	Astable Multivibrator (Clock) Built with TTL ICs	196	
6.4.	Transistor Monostable (One-Shot) Multivibrator Circuits	197	
6.5.	Monostable Multivibrator Integrated Circuit	204	
6.6.	IC Op-Amp Astable Multivibrator	205	
6.7.	IC Op-Amp Monostable Multivibrators	210	
6.8.	555 IC Timer	213	
6.9.	555 Timer as Monostable Multivibrator	217	
6.10.	555 Timer as Astable Multivibrator	220	
6.11.	Astable Blocking Oscillators	223	
6.12.	Monostable Blocking Oscillator (with Emitter Timing)	227	
<b>7.</b>	<b>BISTABLE MULTIVIBRATORS OR FLIP-FLOPS</b>		<b>234</b>
7.1.	Basic Bistable Multivibrator Circuits	234	
7.2.	Flip-Flop Collector Triggering Circuits	238	
7.3.	RS Flip-Flops	242	
7.4.	JK and D Flip-Flops	247	
7.5.	Bistable Multivibrator as Control of Micropower Switch	252	
7.6.	Bistable Control Circuit	257	
<b>8.</b>	<b>BASIC LOGIC GATES AND LOGIC FAMILIES</b>		<b>260</b>
8.1.	Introduction	260	
8.2.	NOR Gates and Nand Gates	261	

**x CONTENTS**

8.3.	Transistor-Transistor Logic (TTL) Circuits	262
8.4.	Emitter-Coupled Logic (ECL) Family	265
8.5.	MOSFET Logic	266
8.6.	Analytic Expressions for MOSFET Characteristics	268
8.7.	Analysis of MOS Inverter Characteristics	271
8.8.	Analysis of CMOS Inverter Characteristics	272
8.9.	Integrated-Injection Logic (I <sup>2</sup> L)	275

**9. DIGITAL COUNTERS, REGISTERS, AND DATA CONVERTERS 280**

9.1.	Counting Chain of $n$ Flip-Flops	280
9.2.	Integrated-Circuit Binary Counters	283
9.3.	Decimal Counters	285
9.4.	Integrated-Circuit BCD Decade Counters	288
9.5.	LCD and LED Seven-Segment Displays	292
9.6.	Scaler (Counter) Control Circuit	297
9.7.	Registers	298
9.8.	Data Converters	302
9.9.	Analog-to-Digital (A/D) Converters (ADCs)	304
9.10.	Digital-to-Analog (D/A) Converters (DACs)	308

**10. LINEAR AND APPROXIMATE RAMP GENERATORS 314**

10.1.	Introduction	314
10.2.	Ramp Generators with Constant Current Sources	315
10.3.	Transistor Bootstrap Ramp Generator	316
10.4.	Integrated Circuit Bootstrap Ramp Generators	317
10.5.	Miller Integrator Using IC Operational Amplifier(s)	322
10.6.	UJT Relaxation Oscillator as Approximate Ramp Generator	324
10.7.	Other Relaxation Oscillators as Approximate Ramp Generators	329

**11. MODULATION, DEMODULATION, AND TIME-DIVISION MULTIPLEXING 336**

11.1.	Introduction to Modulation	336
11.2.	Amplitude Modulation	340

11.3.	AM Detection	343	
11.4.	Frequency Modulation	346	
11.5.	FM Demodulation using a Phase Detector	349	
11.6.	Phase-Locked Loop FM Demodulation	351	
11.7.	Modulation and Demodulation Techniques for PAM, PDM, and PPM	354	
11.8.	Time Division Multiplexing	359	
11.9.	PCM Modulation and Demodulation	365	
11.10.	Digital Modulator for Simultaneous Transmission of Three Signals	369	
11.11.	Modulation and Detection in Optical Fiber Systems		372
11.12.	Data Processing in Multichannel Biotelemetry Systems	377	

## 12. ANALYSIS OF TELEVISION WAVE FORMING AND WAVE PROCESSING CIRCUITS

392

12.1.	Introduction to Television Systems	392	
12.2.	RF Tuner Circuit	400	
12.3.	Oscillator with Automatic Fine Tuning (AFT) System	403	
12.4.	Picture IF Amplifier Circuit	406	
12.5.	Video Detector and Amplifier Circuit	408	
12.6.	Synchronous Separator and Vertical Oscillator Circuit	410	
12.7.	Horizontal AFC and Oscillator Circuit	411	
12.8.	Horizontal Output and High Voltage Circuit	413	
12.9.	Intercarrier Sound and Audio Circuitry in a TV Receiver	415	
12.10.	Introduction to Color Television Systems	419	
12.11.	Principle of Color Television Receivers	423	
12.12.	Integrated Circuits Used in Television	426	
12.13.	Basic TV Terminals	428	
12.14.	TVT Operation Principle	430	

## 13. PULSE-HEIGHT ANALYZERS

442

13.1.	Single-Channel Pulse-Height Analysis	442	
13.2.	Transistor Circuit of Typical Single-Channel Pulse-Height Analyzer	444	

**xii CONTENTS**

13.3.	Single-Channel Pulse-Height Analyzers Built on Linear Integrated Differential Comparators	446
13.4.	Multichannel Pulse-Height Analysis	448
13.5.	Multichannel Pulse-Height Analyzers	453
13.6.	A 100-Channel Pulse Height Analyzer	455

**14. TIME-OF-FLIGHT (TOF) MASS SPECTROMETERS — THE PULSE-TIMING SYSTEMS 465**

14.1.	Introduction	465
14.2.	Basic Principle of TOF Mass Spectrometers	467
14.3.	Electron Multipliers	470
14.4.	Functions in TOF Mass Spectrometry	473
14.5.	Typical Electrometer and Output Circuit	475
14.6.	Typical Pulse Delay Circuit	477
14.7.	Typical Scan Circuit	481
14.8.	High Vacuum Pumps Used in Mass Spectrometers	484

<b>Appendix 1.</b>	<b>Typical Standard Resistor and Capacitor Values</b>	<b>490</b>
--------------------	---	------------

<b>Appendix 2.</b>	<b>Analysis of Periodic Nonsinusoidal Waveforms</b>	<b>492</b>
--------------------	---	------------

<b>Appendix 3.</b>	<b>Glossary</b>	<b>516</b>
--------------------	-----------------	------------

<b>Index</b>	<b>531</b>
--------------	------------