



# Contents

UNIVERSIDAD NACIONAL DE ENTRE RÍOS  
FACULTAD DE INGENIERÍA  
CENTRO DE MEDIOS  
BIBLIOTECA

4 0 1 7 , = page

Device Cross Reference .....	7
Abstracts of Applications Documents .....	11
<b>Applications Documents</b>	
AN433 TV On-Screen Display Using the MC68HC05T1 .....	17
AN438 300W, 88-108MHz Amplifier Using the TP1940 MOSFETs Push-Pull Transistor .....	37
AN531 MC1596 Balanced Modulator .....	41
AN535 Phase-Locked Loop Design Fundamentals .....	55
AN545A Television Video IF Amplifier Using Integrated Circuits .....	67
AN556 Interconnection Techniques for Motorola's MECL 10,000 Series Emitter Coupled Logic .....	79
AN721 Impedance Matching Networks Applied to RF Power Transistors .....	103
AN761 Video Amplifier Design: Know Your Picture Tube Requirements .....	121
AN779 Low-Distortion 1.6 to 30MHz SSB Driver Designs .....	149
AN791 A Simplified Approach to VHF Power Amplifier Design .....	161
AN827 The Technique of Direct Programming by Using a Two-Modulus Prescaler .....	171
AN829 Application of the MC1374 TV Modulator .....	177
AN847 Tuning Diode Design Techniques .....	189
AN860 Power MOSFETs versus Bipolar Transistors .....	197
AN878 VHF MOS Power Applications .....	203
AN879 Monomax: Application of the MC13001 Monochrome Television Integrated Circuit .....	207
AN921 Horizontal APC/AFC Loops .....	219
AN923 800MHz Test Fixture Design .....	239
AN932 Application of the MC1377 Colour Encoder .....	245
AN955 A Cost Effective VHF Amplifier for Land Mobile Radios .....	257
AN969 Operation of the MC145159 PLL Frequency Synthesizer with Analog Phase Detector .....	261
AN980 VHF Narrowband FM Receiver Design Using the MC3362 and the MC3363 Dual Conversion Receivers .....	273
AN1019 Decoding Using the TDA3330, with Emphasis on Cable In/Cable Out Operation .....	287
AN1040 Mounting Considerations for Power Semiconductors .....	295
AN1041 Mounting Procedures for Very High Power RF Transistors .....	315
AN1044 The MC1378 — A Monolithic Composite Video Synchronizer .....	317
AN1051 Transmission Line Effects in PCB Applications .....	331
AN1076 Speeding up Horizontal Outputs .....	399
AN1080 External-Sync Power Supply with Universal Input Voltage Range for Monitors .....	403
AN1103 Using the CR3424 for High Resolution CRT Applications .....	423
AN1106 Considerations in Using the MHW801 and MHW851 Series RF Power Modules .....	427
AN1107 Understanding RF Data Sheet Parameters .....	431
ANE416 MC68HC05B4 Radio Synthesizer .....	447
ANHK02 Low Power FM Transmitter System MC2831A .....	469
ANHK07 A High Performance Manual-Tuned Receiver for Automotive Application Using Motorola ICs MC13021, MC13020 and MC13041 .....	485
EB104 Get 600 Watts RF from Four Power FETs .....	497
EB109 Low Cost UHF Device Gives Broadband Performance at 3.0 Watts Output .....	505
Additional Information .....	511