

CONTENTS

4044 = 50

UNIVERSIDAD NACIONAL DE ENTRE RÍO
FACULTAD DE INGENIERIA
CENTRO DE MEDIOS
BIBLIOTECA

Preface	iv	35. JFET Applications	151
Experiments		36. VMOS Circuits	157
1. Voltage and Current Sources	1	37. The Silicon Controlled Rectifier	163
2. Thevenin's Theorem	5	38. Lower Cutoff Frequencies	167
3. Troubleshooting	9	39. Upper Cutoff Frequencies	171
4. The Diode Curve	13	40. Decibels and Risetime	175
5. Diode Approximations	17	41. The Differential Amplifier	181
6. Rectifier Circuits	21	42. The Operational Amplifier	185
7. The Capacitor-Input Filter	27	43. Noninverting Voltage Feedback	189
8. Voltage Doublers	33	44. Negative Feedback	193
9. Limiters and Peak Detectors	39	45. Gain-Bandwidth Product	199
10. DC Clampers and Peak-to-Peak Detectors	43	46. Linear IC Amplifiers	203
11. Zener Diode	49	47. Current Source and Active Filter	209
12. The Zener Regulator	53	48. Active Diode Circuits and Comparators	215
13. Optoelectronic Devices	57	49. Waveshaping Circuits	221
14. The CE Connection	63	50. The Wien-Bridge Oscillator	227
15. Collector Curves	67	51. The LC Oscillator	231
16. Base Bias	71	52. Unwanted Oscillations	235
17. LED Drivers	75	53. The 555 Timer	239
18. Setting Up a Stable <i>Q</i> Point	79	54. Voltage Regulation	245
19. Biasing PNP Transistors	83	55. Three-Terminal IC Regulators	251
20. Transistor Bias	87		
21. Coupling and Bypass Capacitors	91		
22. AC Emitter Resistance	95	Appendix	
23. The CE Amplifier	99	Parts and Equipment	257
24. Other CE Amplifiers	103	Data Sheets	259
25. Cascaded CE Stages	107	1N753	259
26. AC Load Lines	111	1N914	261
27. Class A Amplifiers	115	1N4001	262
28. The Emitter Follower	119	2N3904	263
29. Class B Push-Pull Amplifiers	123	2N3906	268
30. The Zener Follower	127	2N4444	273
31. An Audio Amplifier	131	MPF102	275
32. JFET Curves	135	LM318	277
33. JFET Bias	139	LM340	281
34. JFET Amplifiers	147	LM741	286