

Analysis and application of analog electronic circuits to biomedical instrumentation – 2nd. Ed.

ISBN 9781439866696

Table of Contents

All chapters include an introduction and chapter summary.

Sources and Properties of Biomedical Signals

Sources of Endogenous Bioelectric Signals

Nerve Action Potentials

Muscle Action Potentials

The Electrocardiogram

Other Biopotentials

Electrical Properties of Bioelectrodes

Exogenous Bioelectric Signals

Properties and Models of Semiconductor Devices Used in Analog Electronic Systems

pn Junction Diodes

Midfrequency Models for BJT Behavior

Midfrequency Models for Field-Effect Transistors

High-Frequency Models for Transistors and Simple Transistor Amplifiers

Photons, Photodiodes, Photoconductors, LEDs, and Laser Diodes

The Differential Amplifier

DA Circuit Architecture

Common-Mode Rejection Ratio

CM and DM Gain of Simple DA Stages at High Frequencies

Input Resistance of Simple Transistor DAs

How Signal Source Impedance Affects the Low-Frequency CMRR

How Op Amps Can be Used to Make DAs for Medical Applications

General Properties of Electronic, Single-Loop Feedback Systems

Classification of Electronic Feedback Systems

Some Effects of Negative Voltage Feedback

Effects of Negative Current Feedback

Positive Voltage Feedback

Feedback, Frequency Response, and Amplifier Stability

Review of Amplifier Frequency Response

What Is Meant by Feedback System Stability

The Use of Root Locus in Feedback Amplifier Design

Use of Root-Locus in the Design of "Linear" Oscillators

Operational Amplifiers and Comparators

The Ideal Op Amp

Practical Op Amps

Gain-Bandwidth Relations for Voltage-Feedback OAs

Gain-Bandwidth Relations in Current Feedback Amplifiers

Analog Voltage Comparators

Some Applications of Op Amps in Biomedicine

Introduction to Analog Active Filters

Active Filter Applications
Types of Analog Active Filters
Electronically Tunable AFs

Instrumentation and Medical Isolation Amplifiers

Instrumentation Amps
Medical Isolation Amps
Safety Standards in Medical Electronic Amplifiers
Medical-Grade Power Supplies

Noise and the Design of Low-Noise Signal Conditioning Systems for Biomedical Applications

Descriptors of Random Noise in Biomedical Measurement Systems
Propagation of Noise Through LTI Filters
Noise Factor and Figure of Amplifiers
Cascaded Noisy Amplifiers
Noise in Differential Amplifiers
Effect of Feedback on Noise
Examples of Noise-Limited Resolution of Certain Signal Conditioning Systems
Some Low-Noise Amplifiers
The Art of Low-Noise Signal Conditioning System Design

Digital Interfaces

Aliasing and the Sampling Theorem
Digital-to-Analog Converters
Sample-and-Hold Circuits
Analog-to-Digital Converters
Quantization Noise

Modulation and Demodulation of Biomedical Signals

Modulation of a Sinusoidal Carrier Viewed in the Frequency Domain
Implementation of AM
Generation of Phase and Frequency Modulation
Demodulation of Modulated Sinusoidal Carriers
Modulation and Demodulation of Digital Carriers

Power Amplifiers and Their Applications in Biomedicine

Power Output Devices
Classes of Power Amplifiers: PA Efficiency
Class D Power Amplifiers
Nonlinearity and Distortion in PAs
IC Voltage Regulators in Medical Electronic Systems
Heatsinking

Wireless Patient Monitoring

Sensors and Sensor Signals Communicated in WPM
Modulation in WPM
RF Communications Protocols Used in WPM
UHF Transmitters and Antennas
WPM Systems
How WPM Reduces the Probability of Patient Microshock
Privacy in WPM

RFID Tags, GPS Tags, and Ultrasonic Tags Used in Ecological Research

Applications of RFID Tags
Design of RFID Tags

Tag Readers
GPS Tags
Ultrasonic Tags in Fisheries Biology

Examples of Special Analog Circuits and Systems Used in Biomedical Instrumentation

The Phase-Sensitive Rectifier
Phase Detectors
Voltage and Current-Controlled Oscillators
Phase-Lock Loops
True RMS Converters
IC Temperature Sensors
Three Examples of Medical Instrumentation Systems

Appendix

Glossary

Bibliography and Recommended Reading