

Contents



UNIVERSIDAD NACIONAL DE ENTRE RÍOS
FACULTAD DE INGENIERIA
CENTRO DE MEDIOS
BIBLIOTECA

№ 1507

Chapter 1	Review of Electronic Devices	3
	Voltages, Currents, Batteries and Current Sources	3
	Resistors, and Voltage Dividers	6
	Capacitors and Inductors	10
	Transformers	13
	Diodes and Zener Diodes	14
	Transistors	17
	Relays	24
	Power Supplies	25
	Integrated Circuit Regulating Modules	28
	Problems	28
	Experiment 1—Conductivity Sensor	33
Chapter 2	Operational Amplifiers and Instrumentation Amplifiers	37
	General Operational Amplifier Applications	37
	Schematic Diagram of Op-amp	39
	Power Supplies for Op-amp	39
	The Ideal Op-amp	40
	Three Basic Rules of Ideal Op-amp Design	41
	Real-World Op-amps	51
	Instrumentation Amplifiers	53
	Common Mode Signals	54
	Commercial, Monolithic Instrumentation Amplifiers	59
	Isolation Amplifiers	60
	Problems	60
	Experiment 2—Construction of a General-Purpose Differential Bioamplifier	65

Chapter 3	Linear Systems Theory	71
	Linearity and Time Invariance	72
	The Impulse Response	75
	Frequency Domain Analysis	76
	Fourier Analysis	79
	General Mathematical Description of Linear Systems	86
	Zero-Order Systems	87
	First-Order Systems	88
	Second-Order Systems	103
	Predicting the Response of a System to an Arbitrary Input Waveform	112
	Laplace Transform Method of Solving Linear Differential Equations	116
	Problems	124
	Experiment 3A—Calibration of Bioamplifier	129
	Experiment 3B—Operational Amplifier Oscillators	130
Chapter 4	Origin of Biopotentials	137
	Free Diffusion of Uncharged Molecule	137
	Diffusion of a Single Ionic Species	141
	Nernst Potentials	142
	Mobilities of Ions	144
	Diffusion of Two Ionic Species: Diffusion Potentials or Liquid Junction Potentials	145
	The Goldman Equation	147
	Electrical Equivalent Circuit Analogy	149
	Problems	152
	Experiment 4A—Diffusion Potentials	154
	Experiment 4B—Ion-selective Membranes	156
Chapter 5	Human Biopotentials	159
	Graded Potentials	159
	Nerve Action Potential	161
	The Evoked Potential	166
	The Electroencephalogram (EEG)	168
	The Electromyogram (EMG)	168
	The Electrocardiogram (ECG)	170
	ECG Electrodes and Measurements	173
	Problems	177
	Experiment 5—Human Biopotentials	178
Chapter 6	Signals and Noise in Biological Systems	181
	Origins of Noise	181
	Characterizing Noise	182

Signal Averaging	185
Electronic Noise Sources, Inherent Noise	186
Interference Noise	189
Negative Capacitance Amplifier	189
Grounding	191
Driven Shields or Guard Rings	193
Problems	194
Chapter 7 Biopotential Electrodes	199
Inserting Metal into Solutions	199
Half-Cell Potentials	200
Passing Currents through Electrodes	203
Electrode Equivalent Circuits	205
Electrode Polarization	205
Real-World Polarizable and Nonpolarizable Electrodes	208
Microelectrodes	209
Glass Microelectrodes	211
Metal Microelectrodes	215
Microelectrodes in Neuroprostheses	217
Problems	217
Experiment 7—Biopotential Electrodes	220
Chapter 8 Ion-Sensitive, Potentiometric, and Amperometric Electrodes	223
Amperometric and Potentiometric Sensors	224
Ion-Sensitive Electrodes	224
pH Electrodes	230
Liquid Ion Exchanger Potentiometric Electrodes	231
Solid-State Potentiometric Electrodes	232
Chemfet Ion-Selective Electrodes	232
Amperometric Electrodes	233
Oxygen Electrodes	234
Enzyme Electrodes	237
Problems	239
Experiment 8—The Oxygen Electrode	240
Chapter 9 Mechanical Transducers	243
Displacement Transducers	244
Force Transducers	250
Blood Pressure Measurements	254
Problems	261
Experiment 9—Physiology of Muscle as Studied with a Force Transducer	263

Chapter 10 Temperature Transducers	267
Thermistors	267
How Do Thermistor Work?	269
Current-Voltage Relation of a Thermistor	271
Thermistor Linearization	274
Semiconductor Integrated Circuit Temperature Sensors	275
Thermocouple Temperature Sensors	277
Problems	278
Experiment 10—The Thermistor	279
Chapter 11 Light and Spectrophotometry	283
Light	283
Dual Nature of Light	284
Interaction of Light with Matter	286
Absorption Spectra	286
Laws of Light Absorption	287
Spectrophotometers	290
Light Sources	290
Wavelength Selectors	295
Photodetectors	298
The Optoisolator	302
Problems	304
Experiment 11—Laws of Photometry, Photodiodes, and LEDs	306
Chapter 12 Measurement of Liquid and Gas Flows	309
Electromagnetic Flowmeters	309
Ultrasonic Flowmeters	314
Dye Dilution Flowmeters	326
Respiratory Volumes and Velocities: Measurements of Gas Flow	330
Gas Flowmeters	333
Problems	337
Experiment 12A—Dye Dilution Cardiac Output Determinations	339
Experiment 12B—Measurement of Gas Flows during Respiratory Maneuvers	341
Chapter 13 Analog Linearization	345
Linearization (or Curve Fitting) in Research Applications	351
Modeling a Data Set with an Equation	351
Modeling an Equation with an Analog Circuit	354
Multifunction Modules	357

Contents

xiii

Problems	359
Experiment 13-Analog Linearization	362
Chapter 14 Review of Digital Electronic Devices	371
A Few Definitions	371
Why Use Two-State Logic?	373
Alternative Number Representations	373
Bits, Nibbles, and Bytes	376
Logic Gates	377
Decoding	381
Tristate Buffers	383
Latches	387
Flip-Flops	388
Problems	394
Experiment 14 Digital Devices	397
Chapter 15 Talking to Computers	401
Talking to a Computer: The Programming Language	403
Programming in BASIC	405
The BASIC Vocabulary	409
Graphics Commands	418
Editing BASIC Programs on the IBM PC/XT	421
Problems	423
Experiment 15—Programming in BASIC	425
Chapter 16 Interfacing Computers to the Outside World	427
Addresses and Data	427
Talking to IBM PC/XT through Input-Output Channels	430
Memory versus Input-Output	432
INP and OUT	432
Peripheral Interface Adapter (PIA) or the Programmable Peripheral Interface	435
Bit Masks	441
A/D and D/A Converters	443
The D/A Converter	444
Analog-to-Digital Conversion	447
Problems	454
Experiment 16 Computer Control and Data Acquisition	455
Chapter 17 Digital Signal Processing	459
Data Set and Data Storage	460
Looking at Our Data	462

Storing and Retrieving Data from a Floppy Disk	463
Low-Pass Smoothing Filters	465
Least-Mean-Square Filters	471
Convolution	475
Problems	478
Experiment 17—Making a Digital Oscilloscope IBM PC/XT	479

Chapter 18 Safety in Bioinstrumentation 481

Pervasiveness of Electricity and of Electrical Shock	482
Electrical Outlet: Hot, Neutral, and Ground Connections	483
Effects of Electrical Current on Human Body	484
Hazards of Microshock	485
Techniques to Reduce Electrical Shock	486
Bring a Concept to the Marketplace: A Case Study	491

Appendix Data Sheets

A.1 2N3904 Transistor	498
A.2 Crydom Solid-State Relay	499
A.3 LM117 3-Terminal Adjustable Voltage Regulator	500
A.4 TL062 Operational Amplifier	502
A.5 AD545 FET-Input Operational Amplifier	505
A.6 AD522 Instrumentation Amplifier	509
A.7 3450 Isolation Amplifier	513
A.8 LM555 Timer	518
A.9 Ultra Bright Light-Emitting Diodes	523
A.10 Pin Photodiodes	525
A.11 Dual Optocoupler	527
A.12 AD534 Multifunction Module	529
A.13 74LS90 Decade and Binary Counters	535
A.14 DAC0800 Digital-to-Analog Converter	540
A.15 ADC0809 Analog-to-Digital Converter	545