

Table of Contents

SECTION	TITLE	PAGE
■ Product Features		
■ IC Selection Guides		
	CSC Power Supply Control IC Selection Guide	
	CSC Linear Regulator Selection Guide	
■ Power Conversion IC Cross Reference Index		
■ Regulators		
Single Output Linear Regulators		
CS-403	5V, 500mA Low Dropout Linear Regulator with RESET	1
CS-8120	5V, 300mA Low Dropout Regulator with RESET and ENABLE	5
CS-8121	5V, 1A Low Dropout Linear Regulator with RESET and ENABLE	11
CS-8125	5V, 750mA Low Dropout Linear Regulator with Delayed RESET	17
CS-8128	5V Linear Controller/Driver	23
CS-8129	5V, 500mA Low Dropout Linear Regulator with Lower RESET Threshold	29
CS-8140, CS-8141	5V, 500mA Low Dropout Linear Regulator with ENABLE, RESET, and WATCHDOG	35
CS-925A	5V, 750mA Low Dropout Linear Regulator with Delayed RESET	43
Dual Output Linear Regulators		
CS-8109	12V Linear Flash EPROM Programming Regulator and 2.5V Precision Reference	51
CS-8135	5V, 5V Low Dropout Dual Regulator with RESET/ENABLE	57
CS-8145	10V, 5V Low Dropout Dual Regulator with ENABLE	63
CS-8147	10V, 5V Low Dropout Dual Regulator with ENABLE	69
CS-8154	12V, 5V Low Dropout Dual Regulator with ENABLE	71
CS-8155	12V, 5V Low Dropout Dual Regulator with ENABLE	73
CS-8156	12V, 5V Low Dropout Dual Regulator with ENABLE	79
CS-8158	12V, 5V Low Dropout Dual Regulator with ENABLE	85
CS-8164	8V, 5V Low Dropout Dual Regulator with ENABLE	87
CS-8165	8V, 5V Low Dropout Dual Regulator with ENABLE	89
Switching Regulators		
CS-3970	5A High Efficiency Switching Regulator	97
CS-3971	2.5A High Efficiency Switching Regulator	99
CS-3972	1.25A High Efficiency Switching Regulator	101
CS-3980	5A High Efficiency Switching Regulator	103
CS-3981	2.5A High Efficiency Switching Regulator	105
CS-3982	1.25A High Efficiency Switching Regulator	107
■ Power Supply Control ICs		
Voltage Mode PWM Control		
CS-3524A	Voltage Mode PWM Control Circuit with 200mA Output Drivers	111
Current Mode PWM Control		
CS-2841B	Automotive Current Mode PWM Control Circuit	119
CS-2842A, CS-2843A, CS-3842A, CS-3843A	Off-Line Current Mode PWM Control Circuit with Undervoltage Lockout	125
CS-2844, CS-2845, CS-3844, CS-3845	Current Mode PWM Control Circuit with 50% Max Duty Cycle	131
CS-320, CS-321	1MHz Current-Mode Control IC	137

Table of Contents: continued

SECTION	TITLE	PAGE
■ Power Supply Control ICs (continued)		
Current Mode PWM Control (continued)		
CS-322, CS-324	Hysteretic Current-Mode Controller	143
CS-323, CS-325	Hysteretic Current-Mode Controller	147
CS-3865	High Performance Dual Channel Current Mode Controller	149
Resonant Mode PWM Control		
CS-360	1MHz Resonant-Mode Control	159
CS-361	2MHz Resonant-Mode Control	171
Auxiliary ICs		
CS-3810	Power Factor Correction	181
CS-3706	Dual Output Driver	189
■ Power Conversion Support Circuits		
CS-1009	2.5 Volt Reference	195
CS-2516	Pulse-Load Battery Monitor	199
■ Power Conversion Application Notes		
	Control IC for Near Unity Power Factor in SMPS	207
	Single CS-3842A Provides Control for 500W/200kHz Current-Mode Power Supply	213
	Advantages of Variable Frequency Operation Using the 1MHz CS-320 Current-Mode Controller	223
	Half-Bridge Resonant Converter using the CS-360	231
■ Package Information		
	Mechanical Package Specifications	A-1
	ASIC Flip Chips: Manufacture and Use	A-13



UNIVERSIDAD NACIONAL DE ENTRE RÍOS
 FACULTAD DE INGENIERIA
 CENTRO DE MEDIOS
 BIBLIOTECA

Nº 3129