

# Linear Applications Numerical List

4026

UNIVERSIDAD NACIONAL DE ENTRE RIOS  
FACULTAD DE INGENIERIA  
CENTRO DE MEDICION  
BIBLIOTECA

APPLICATION NOTES	DATE	REVISION	DATE	PAGE
AN-3 Drift Compensation Techniques for Integrated DC Amplifiers	11/67		6/86	1
AN-4 Monolithic Op Amp—The Universal Linear Component	4/68		6/86	6
AN-13 Application of the LH0002 Current Amplifier	9/68		6/86	16
AN-20 An Application Guide for Op Amps	8/80		6/86	20
AN-21 Designs for Negative Voltage Regulators	12/68		—	32
AN-23 The LM105—An Improved Positive Regulator	1/69		—	41
AN-24 A Simplified Test Set for Op Amp Characterization	1/86		6/86	49
AN-29 IC Op Amp Beats FETs on Input Current	12/69		6/86	59
AN-30 Log Converters	11/69		—	76
AN-31 Op Amp Circuit Collection	2/78		6/86	80
AN-32 FET Circuit Applications	2/70		6/86	105
AN-38 Applications of MOS Analog Switches	1/70		6/86	119
AN-41 Precision IC Comparator Runs for +5V Logic Supply	10/70		—	129
AN-42 IC Provides On-Card Regulation for Logic Circuits	2/71		—	135
AN-46 The Phase Locked Loop IC as a Communications System Building Block	6/71		6/86	141
AN-48 Applications for a New Ultra-High Speed Buffer	8/71		—	155
AN-49 Pin Diode Drivers	1/75		—	162
AN-56 1.2 Volt Reference	12/71		—	168
AN-63 New Design Techniques for FET Op Amps	1/75		—	172
AN-64 LM381 Low Noise Dual Preamplifier	5/72		—	183
AN-69 LM380 Power Audio Amplifier	12/72		—	195
AN-71 Micropower Circuits Using the LM4250 Programmable Op Amp	7/72		—	202
AN-72 The LM3900—A New Current-Differencing Quad + Input Amplifiers	9/72		6/86	211
AN-74 LM139/LM239/LM339—A Quad of Independently Functioning Comparators	1/73		—	256
AN-75 Applications for a High Speed FET Input Op Amp	12/72		—	273
AN-79 IC Pre-Amp Challenges Choppers on Drift	2/73		—	280
AN-81 LM1800 (LM1310, LM1310E) Phase Locked Loop FM Stereo Demodulator	6/73		6/86	288
AN-82 LM125/LM126/LM127 Precision Dual-Tracking Regulators	8/80		6/86	306
AN-87 Comparing the High Speed Comparators	6/73		—	322
AN-88 CMOS Linear Applications	7/73		6/86	328
AN-97 Versatile Timer Operates from Microseconds to Hours	12/73		—	331
AN-103 LM340 Series Three Terminal Positive Regulators	8/80		—	343
AN-104 Noise Specs Confusing?	5/74		6/86	355
AN-110 Fast IC Power Transistor with Thermal Protection	5/74		—	362
AN-115 Wide Range Function Generator	7/74		—	369
AN-116 Use the LM158/258/358 Dual, Single Supply Op Amp	8/80		6/86	374
AN-127 LM143 Monolithic High Voltage Operation Amplifier Applications	4/76		—	378
AN-146 FM Remote Speaker System	6/75		6/86	390
AN-147 Low Cost IC Stereo Receiver	6/75		6/86	394
AN-154 1.3V IC Flasher, Oscillator, Trigger or Alarm	12/75		—	398
AN-156 Specifying A/D and D/A Converters	2/76		6/86	413
AN-161 IC Voltage Reference Has 1 ppm per Degree Drift	6/76		—	419
AN-162 LM2907 Tachometer/Speed Switch Building Block Applications	6/76		6/86	425
AN-173 IC ZXener Eases Reference Design	11/76		—	442
AN-178 Applications for an Adjustable IC Power Regulator	1/77		—	445
AN-180 RMS Converters and Their Applications	12/70		—	449
AN-181 3-Terminal Regulator is Adjustable	3/77		—	453
AN-182 Improving Power Supply Reliability with IC Power Regulators	4/77		—	459
AN-184 References for A/D Converters	7/77		—	462
AN-193 Single Chip Data Acquisition System Amplifiers Analog to Digital Conversion	7/77		—	466
AN-200 CMOS A/D Converter Chips Easily Interface to 8080A Microprocessor System	3/78		—	469

# Linear Applications Numerical List (Continued)

APPLICATION NOTES	REVISION		
	DATE	DATE	PAGE
AN-202 A Digital Multimeter Using ADD3501 .....	7/80	6/86	479
AN-210 New Phase-Locked Loops Have Advantage as Frequency to Voltage Converters (and more) .....	4/79	—	483
AN-211 New Op Amp Ideas .....	12/78	—	491
AN-222 Super Matched Bipolar Transistor Pair Sets New Standard for Drift and Noise .....	7/79	—	517
AN-225 IC Temperature Sensor Provides Thermocouple Cold-Junction Compensation .....	4/79	—	527
AN-227 Applications of Wideband Buffers .....	10/79	—	533
AN-233 The A/D Easily Allows Many Unusual Applications .....	1/80	—	549
AN-236 An Introduction to Sampling Theorem .....	1/80	6/86	554
AN-237 Convolution: Digital Signal Processing .....	1/80	6/86	566
AN-240 Wide-Range Current-to-Frequency Converters .....	5/80	6/86	574
AN-241 Working with High Impedance Op Amps .....	2/80	—	580
AN-242 Applying a New Precision Op Amp .....	4/80	—	586
AN-244 Fiber Optic Applications .....	5/80	—	608
AN-245 Application of the ADC-1210 CMOS A/D Converter .....	—	6/86	618
AN-247 Using the ADC0808/ADC0809 8-Bit $\mu$ P Compatible A/D Converters with 8- Channel Analog Multiplexer .....	9/80	6/86	626
AN-252 Speech Synthesis .....	12/80	6/86	642
AN-253 LH0024 and LH0032 High Speed Op Amp Applications .....	/80	—	654
AN-255 Power Spectrum Estimation .....	11/80	—	665
AN-256 Circuitry for Inexpensive Relative Humidity Measurement .....	8/81	—	693
AN-258 Data Acquisition Using the ADC0816 and ADC0817 8-Bit A/D Converter with On- Chip 16 Channel Multiplexer .....	1/81	6/86	697
AN-260 A 20-Bit (1 ppm) Linear Slope-Integrating A/D Converter .....	1/81	—	719
AN-261 Low Distortion Wideband Power Op Amp .....	7/81	—	725
AN-262 Applying Dual and Quad FET Op Amps .....	5/81	6/86	734
AN-263 Sine Wave Generation Techniques .....	3/81	6/86	741
AN-264 Application of Audio Amplifier Transistor Array ICs .....	5/81	6/86	753
AN-265 An Electronic Watt-Watt Hour Meter .....	2/84	6/86	758
AN-266 Circuit Applications of Sample-Hold Amplifiers .....	1/81	6/86	763
AN-269 Circuit Applications of Multiplying CMOS A/D Converters .....	9/81	6/86	771
AN-271 Applying the New CMOS MICRO-DAC .....	9/81	6/86	776
AN-272 Op Amp Booster Designs .....	9/81	6/86	786
AN-274 CMOS A/D Converter Interfaces Easily with Many Microprocessors .....	7/81	6/86	793
AN-275 CMOS D/A Converters Match Most Microprocessors .....	7/81	—	797
AN-276 A New Low-Cost Sampled Data 10-Bit CMOS A/D Converter .....	7/81	—	802
AN-277 The New MICRO-DAC Product Line for Microprocessor Systems .....	7/81	6/86	807
AN-278 Designing with a New Super Fast Dual Norton Amplifier .....	9/81	6/86	813
AN-280 A/D Converters Easily Interface with 70 Series Microprocessors .....	11/81	—	820
AN-281 Data Acquisition Using INS8048 .....	11/81	6/86	826
AN-284 Single-Supply Applications of CMOS MICRO-DACs .....	9/81	6/86	831
AN-285 An Acoustic Transformer Powered Super-High Isolation Amplifier .....	10/81	6/86	835
AN-286 Applications of the LM392 Comparator Op Amp IC .....	9/81	6/86	839
AN-287 Voice Recording Techniques for Speech Synthesis .....	9/82	6/86	845
AN-288 System-Oriented DC-DC Conversion Techniques .....	4/82	6/86	849
AN-289 Circuit Applications of Analog Data Multiplexers .....	1/82	6/86	854
AN-292 Applications of the LM3524 Pulse-Width-Modulator .....	8/82	6/86	861
AN-293 Control Applications of CMOS DACs .....	3/82	6/86	866
AN-294 Special Sample and Hold Techniques .....	4/82	6/86	872
AN-295 A High Performance Industrial Weighing System .....	3/82	6/86	876
AN-298 Isolation Techniques for Signal Conditioning .....	5/82	6/86	880

# Linear Applications Numerical List (Continued)

APPLICATION NOTES	REVISION		
	DATE	DATE	PAGE
AN-299 Audio Applications of Linear Integrated Circuits .....	4/82	6/86	887
AN-300 Simple Circuit Detects Loss of 4–20 mA Signal .....	5/82	—	892
AN-301 Signal Conditioning for Sophisticated Transducers .....	1/82	—	896
AN-307 Introducing the MF 10: A Versatile Monolithic Active Filter Building Block .....	8/82	—	908
AN-311 Theory and Applications of Logarithmic Amplifiers .....	7/82	—	919
AN-336 Understanding Integrated Circuit Package Power Capabilities .....	3/83	—	924
AN-343 LH1605 Switching Regulator .....	9/83	6/86	929
AN-344 LF13006/LF13007 Precision Digital Gain Set Applications .....	3/84	6/86	939
AN-346 High-Performance Audio Applications of the LM883 .....	8/85	—	944
AN-360 An Auto-Error Correction, Auto-Gain Ranging Analog Data Acquisition System .....	2/84	6/86	953
AN-381 An AM Radio I/C for Electronically Tuned Radios .....	10/84	—	960
AN-382 AM and FM Integrated Circuits for Electronically Tuned Radios .....	1/85	—	973
AN-384 Audio Noise Reduction and Masking .....	3/85	—	987
AN-386 A Non-Complementary Audio Noise Reduction System .....	3/85	—	993
AN-390 DNR "TM" Applications of the LM1894 .....	3/85	—	1003
AN-391 The LM1893: A High Quality TV Video I.F. Amplifier and Synchronous Detector for Cable Receivers .....	3/85	—	1012
AN-402 LM2889 R.F. Modulator .....	6/85	6/86	1028
AN-407 DC Coupled Tape Head Pre-Amplifiers .....	6/85	—	1039
AN-428 Preserving and Verifying the LF400's Fast Setting Time .....	12/85	—	1046
AN-435 LMC835 Digital Controlled Graphic Equalizer .....	3/86	—	1052
AN-446 A 150W IC Op Amp Simplifies Design of Power Circuits .....	4/86	—	1060
AN-447 Protection Schemes for BIFET Amplifiers and Switches .....	4/86	—	1074
AB-7 Multivibrator Timer CAD .....	3/86	—	1077
AB-10 Fluid Level Control System .....	11/83	—	1079
AB-11 High-Efficiency Regulator Has Low Drop-Out Voltage .....	9/83	6/86	1081
AB-12 Wide Adjustable Range PNP Voltage Regulator .....	2/84	—	1082
AB-20 Electrostatic Transducer Provides Wide Range Ultrasonic Measurement .....	10/85	6/86	1083
AB-24 Bench Testing LM3900 and LM359 Input Parameters .....	12/85	—	1085
AB-25 Dithering Display Expands Bar Graph's Resolution .....	8/81	—	1087
LB-1 Instrumentation Amplifier .....	3/69	—	1089
LB-2 Feedforward Compensation Speeds Op Amps .....	3/69	—	1091
LB-3 Worst Case Power Dissipation in Linear Regulators .....	3/69	—	1093
LB-4 Fast Compensation Extends Power Bandwidth .....	4/69	—	1095
LB-5 High Q Notch Filter .....	3/69	—	1096
LB-6 Fast Voltage Comparators with Low Input Current .....	5/69	—	1097
LB-7 Tracking Voltage Regulators .....	8/69	6/86	1100
LB-8 Precision AC/DC Converters .....	8/69	—	1103
LB-9 Universal Balancing Techniques .....	8/69	—	1105
LB-10 IC Regulators Simplify Power Supply Design .....	1/70	—	1107
LB-11 The LM110—An Improved IC Voltage Follower .....	3/70	—	1109
LB-12 An IC Voltage Comparator for High Impedance Circuitry .....	1/70	—	1112
LB-14 Speed Up the LM108 with Feedforward Compensation .....	11/70	—	1114
LB-15 High Stability Regulators .....	1/71	—	1116
LB-16 Easily Tuned Sine Wave Oscillators .....	3/71	—	1118
LB-17 LM118 Op Amp Slews 70V/ $\mu$ sec .....	9/71	—	1120
LB-18 +5V to -15V DC Converter .....	7/72	—	1122
LB-19 Predicting Op Amp Slew Rate Limited Response .....	8/72	—	1124
LB-20 A Fully Differential Input Voltage Amplifier .....	12/72	—	1126
LB-21 Instrumentational Amplifier .....	6/73	—	1128
LB-22 Low Drift Amplifier .....	3/86	—	1130

# Linear Applications Numerical List (Continued)

APPLICATION NOTES		DATE	REVISION	PAGE
			DATE	
LB-23	Precise Tri-Wave Generation .....	6/73	—	1131
LB-24	Versatile IC Pre-Amp Makes Thermocouple Amplifier with Cold Junction Compensation .....	6/73	—	1132
LB-25	True rms Detector .....	6/73	—	1134
LB-26	Specifying Selected Op Amps and Comparators .....	10/73	—	1136
LB-27	Micropower Thermometer .....	1/74	—	1138
LB-28	General Purpose Power Supply .....	6/74	—	1140
LB-29	Low Cost AM Radio System Using LM1820 and LM386 .....	2/75	6/86	1142
LB-32	Microvolt Comparator .....	6/76	—	1145
LB-34	A Micropower Voltage Reference .....	6/76	—	1147
LB-35	Adjustable 3-Terminal Regulator for Low-Cost Battery Charging Systems .....	8/76	—	1148
LB-37	Low Current Ammeter .....	2/77	—	1150
LB-38	Wide Range Timer .....	2/77	—	1151
LB-39	Circuit Techniques for Avoiding Oscillations in Comparator Applications .....	1/78	—	1152
LB-40	Two Wire Current Transmitters .....	12/78	6/86	1154
LB-41	Precision Reference Uses Only Ten Microamperes .....	6/78	—	1156
LB-42	Get Fast Stable Response from Improved Unity-Gain Followers .....	8/78	—	1158
LB-44	Get More Power Out of Dual or Quad Op Amps .....	4/79	—	1160
LB-45	Frequency-to-Voltage Converter Uses Sample-and-Hold to Improve Response and Ripple .....	4/79	—	1162
LB-46	A New Production Technique for Trimming Voltage Regulators .....	7/79	6/86	1164
LB-47	High Voltage Adjustable Power Supplies .....	3/80	—	1166
LB-48	Simple Voltmeter Monitors TTL Supplies .....	2/80	—	1168
LB-49	Programmable Power Regulators Help Check Out Computer System Operating Margins .....	1/85	—	1170
LB-51	Add Kelvin Sensing and Parallel Capability to 3-Terminal Regulators .....	3/81	—	1172
LB-52	A Low Noise Precision Op Amp .....	12/80	—	1174
LB-53	$\mu$ P Interface for a Free Running A/D Allows Asynchronous Reads .....	7/81	6/86	1176
LB-54	Circuit for Evaluation of Custom Vocabulary EPROM Prototype Set .....	6/81	6/86	1178
Appendix A	The Monolithic Operational Amplifier: A Tutorial Study .....	12/84	6/86	1180
Appendix B	A Color TV Primer for the E.E. ....	10/85	—	1201
Appendix C	V/F Converter IC's Handle Frequency-to-Voltage Needs .....	8/80	6/86	1207
Appendix D	Versatile Monolithic V/F's Can Compute as well as Convert with High Accuracy .....	8/80	6/86	1213
Appendix E	Standard Resistance Values .....	6/86	—	1220